

# HW3 (Programming Part) Report

In case VSCode does not render this markdown file correctly, please refer to `report.pdf` for correctly rendered content.

## Design

### ALU Module

The value of `data_o` is defined in behavioral level, that is, the output signal is event-driven. Whenever any of the signals `ALUctrl_i`, `data1_i`, or `data2_i` changes, `data1_i (op) data2_i` is calculated based on the value of `ALUctrl_i` and passed to register `data_o`. It is worth noting that wires and registers are unsigned by default; to apply an arithmetic right shift (`>>>` in Verilog) to `data1_i` in the case `ALUctrl_i == 110`, `data1_i` (unsigned) has to be casted to its signed value first. That's why in line 24 of `ALU.v` I use `$signed` function to cast `data1_i`.

In addition, a default case is added in lines 27~28 of `ALU.v` to ensure `data_o` is assigned some value in case the value of `ALUctrl_i` is not covered by cases above. However, all the 8 possible values of `ALUctrl_i` are listed in the `case` statement so the default case is redundant.

The value of `zero_o` is defined in register transfer level (RTL). Whenever register `data_o` changes its value, that value is compared with `0`, and the resultant bit (indicating whether `data_o` is zero or not) is passed to wire `zero_o`.

### Registers Module

The functionality of `Registers` module can be split into reading from registers and writing to a register.

#### Read from registers

First, I define a macro `read_reg(addr)` to check whether the register to read from is register 0. If `addr` is `0`, meaning a read from register 0, then it returns `32'b0`, which is hard-coded in the program as the register should be hardwired to zero. Otherwise, we are reading from a register that is not register 0, so we can simply obtain the value by `registers[addr]`.

Then, I define the values of wire `RS1data_o` and `RS2data_o` in RTL by connecting each wire

to the corresponding wire that stores the address of the register to read (namely

`RS1addr_i` and `RS2addr_i`) via `read_reg` macro.

## Write to register

This functionality is defined in behavioral level. On the rising edge of the clock signal (`clk_i`), if `RegWrite_i == 1` and the register to write to is not register 0, then store the value of `RDdata_i` into register `registers[RDaddr_i]`. Note that we check the register address here before performing the write to ensure that register 0 is not written.

## Testing

---

### ALU Module

I used the module `ALU_tb` in `ALU_tb.v` as the testbench for `ALU` module. `ALU_tb` will first instantiate the `ALU` module and then repeatedly test `ALU` using a loop.

In each iteration of the loop, the values for the ALU inputs `data1_i` and `data2_i` are randomly generated and the correct result (the expected value of `data_o`) is calculated using Verilog code; then, after waiting for some time units for the signals in `ALU` to propagate, the values of `data_o` and `zero_o` are compared to their expected values. If there are no errors found in the end, `all correct!` is printed.

### Testing Commands

1. Compile the testbench:

```
1 | iverilog -o ALU_tb.vvp ALU_tb.v ALU.v
```

2. Execute the testbench:

```
1 | vvp ALU_tb.vvp
```

3. View the resultant waveforms:


```
1 | gtkwave ALU_tb.vcd --rcvar 'do_initial_zoom_fit yes'
```

### Test Results

- Testbench output:

```
>>> ~/ntu/computer-architecture/hw/hw3-programming vvp ALU_tb.vvp
VCD info: dumpfile ALU_tb.vcd opened for output.
@0: data1 = xxxxxxxx, data2 = xxxxxxxx, ALUctrl = xxx, data = xxxxxxxx, zero = x
@10: data1 = 12153524, data2 = 12153524, ALUctrl = 001, data = 00000000, zero = 1
@30: data1 = c0895e81, data2 = 8484d609, ALUctrl = 000, data = 450e348a, zero = 0
@50: data1 = b1f05663, data2 = 06b97b0d, ALUctrl = 000, data = b8a9d170, zero = 0
@70: data1 = 46df998d, data2 = b2c28465, ALUctrl = 001, data = 941d1528, zero = 0
@90: data1 = 89375212, data2 = 00f3e301, ALUctrl = 001, data = 88436f11, zero = 0
@110: data1 = 06d7cd0d, data2 = 3b23f176, ALUctrl = 010, data = 0203c104, zero = 0
@130: data1 = 1e8dcd3d, data2 = 76d457ed, ALUctrl = 010, data = 1684452d, zero = 0
@150: data1 = 462df78c, data2 = 7cfde9f9, ALUctrl = 011, data = 7efdfbfd, zero = 0
@170: data1 = e33724c6, data2 = e2f784c5, ALUctrl = 011, data = e3f7a4c7, zero = 0
@190: data1 = d513d2aa, data2 = 72aff7e5, ALUctrl = 100, data = a7bc254f, zero = 0
@210: data1 = bbd27277, data2 = 8932d612, ALUctrl = 100, data = 32e0a465, zero = 0
@230: data1 = 47ecdb8f, data2 = 793069f2, ALUctrl = 101, data = 6e3c0000, zero = 0
@250: data1 = e77696ce, data2 = f4007ae8, ALUctrl = 101, data = 7696ce00, zero = 0
@270: data1 = e2ca4ec5, data2 = 2e58495c, ALUctrl = 110, data = fffffefe, zero = 0
@290: data1 = de8e28bd, data2 = 96ab582d, ALUctrl = 110, data = fffff471, zero = 0
@310: data1 = b2a72665, data2 = b1ef6263, ALUctrl = 111, data = 1654e4cc, zero = 0
@330: data1 = 0573870a, data2 = c03b2280, ALUctrl = 111, data = 0573870a, zero = 0
all correct!
ALU_tb.v:85: $finish called at 34000 (10ps)
```

- Waveforms:

 

## Registers Module

I used the module `Registers_tb` in `Registers_tb.v` as the testbench for `Registers` module. `Registers_tb` will first instantiate the `Registers` module and then repeatedly test `Registers` using a loop.

In each iteration of the loop, 2 registers, say, registers `i` and `j`, are chosen among all 32 registers. Then on the falling edge of the clock signal, we write a random 32-bit value to register `i`. On the next falling edge, we read from register `i` and check whether the value read matches the value previously written to register `i`, and then we write another random value to register `j`. On the next falling edge, we read from register `j` and check whether the value read matches the value previously written to register `j`. In addition, we also set `RegWrite_i` to 0 and try to write a value different from the one currently stored in register `j`, and then check if the new value has been successfully written by reading register `j` at the next falling edge.

If there are no errors found in the end, `all correct!` is printed.

## Testing Commands

1. Compile the testbench:

```
1 | iverilog -o Registers_tb.vvp Registers_tb.v Registers.v
```

## 2. Execute the testbench:

```
1 | vvp Registers_tb.vvp
```

## 3. View the resultant waveforms:

```
1 | gtkwave Registers_tb.vcd --rcvar 'do_initial_zoom_fit yes'
```

## Test Results

- Testbench output (excerpt):

```
>>> ~/ntu/computer-architecture/hw/hw3-programming vvp Registers_tb.vvp
VCD info: dumpfile Registers_tb.vcd opened for output.
@0: RS1addr = x, RS2addr = x, RDaddr = x, RDdata = xxxxxxxx, RegWrite = x, RS1data = xxxxxxxx, RS2data = xxxxxxxx
@10: RS1addr = 0, RS2addr = 1, RDaddr = 0, RDdata = 12153524, RegWrite = 1, RS1data = 00000000, RS2data = xxxxxxxx
@20: RS1addr = 0, RS2addr = 1, RDaddr = 1, RDdata = c0895e81, RegWrite = 1, RS1data = 00000000, RS2data = xxxxxxxx
@25: RS1addr = 0, RS2addr = 1, RDaddr = 1, RDdata = c0895e81, RegWrite = 1, RS1data = 00000000, RS2data = c0895e81
@30: RS1addr = 0, RS2addr = 1, RDaddr = 1, RDdata = c0895e82, RegWrite = 0, RS1data = 00000000, RS2data = c0895e81
@50: RS1addr = 0, RS2addr = 2, RDaddr = 0, RDdata = 8484d609, RegWrite = 1, RS1data = 00000000, RS2data = xxxxxxxx
@60: RS1addr = 0, RS2addr = 2, RDaddr = 2, RDdata = b1f05663, RegWrite = 1, RS1data = 00000000, RS2data = xxxxxxxx
@65: RS1addr = 0, RS2addr = 2, RDaddr = 2, RDdata = b1f05663, RegWrite = 1, RS1data = 00000000, RS2data = b1f05663
@70: RS1addr = 0, RS2addr = 2, RDaddr = 2, RDdata = b1f05664, RegWrite = 0, RS1data = 00000000, RS2data = b1f05663
@90: RS1addr = 0, RS2addr = 3, RDaddr = 0, RDdata = 06b97b0d, RegWrite = 1, RS1data = 00000000, RS2data = xxxxxxxx
@100: RS1addr = 0, RS2addr = 3, RDaddr = 3, RDdata = 46df998d, RegWrite = 1, RS1data = 00000000, RS2data = xxxxxxxx
@105: RS1addr = 0, RS2addr = 3, RDaddr = 3, RDdata = 46df998d, RegWrite = 1, RS1data = 00000000, RS2data = 46df998d
@110: RS1addr = 0, RS2addr = 3, RDaddr = 3, RDdata = 46df998e, RegWrite = 0, RS1data = 00000000, RS2data = 46df998d
@130: RS1addr = 0, RS2addr = 4, RDaddr = 0, RDdata = b2c28465, RegWrite = 1, RS1data = 00000000, RS2data = xxxxxxxx
@140: RS1addr = 0, RS2addr = 4, RDaddr = 4, RDdata = 89375212, RegWrite = 1, RS1data = 00000000, RS2data = xxxxxxxx
@145: RS1addr = 0, RS2addr = 4, RDaddr = 4, RDdata = 89375212, RegWrite = 1, RS1data = 00000000, RS2data = 89375212
@150: RS1addr = 0, RS2addr = 4, RDaddr = 4, RDdata = 89375213, RegWrite = 0, RS1data = 00000000, RS2data = 89375212
@170: RS1addr = 0, RS2addr = 5, RDaddr = 0, RDdata = 00f3e301, RegWrite = 1, RS1data = 00000000, RS2data = xxxxxxxx
@180: RS1addr = 0, RS2addr = 5, RDaddr = 5, RDdata = 06d7cd0d, RegWrite = 1, RS1data = 00000000, RS2data = xxxxxxxx
@185: RS1addr = 0, RS2addr = 5, RDaddr = 5, RDdata = 06d7cd0d, RegWrite = 1, RS1data = 00000000, RS2data = 06d7cd0d
@190: RS1addr = 0, RS2addr = 5, RDaddr = 5, RDdata = 06d7cd0e, RegWrite = 0, RS1data = 00000000, RS2data = 06d7cd0d
@210: RS1addr = 0, RS2addr = 6, RDaddr = 0, RDdata = 3b23f176, RegWrite = 1, RS1data = 00000000, RS2data = xxxxxxxx
@220: RS1addr = 0, RS2addr = 6, RDaddr = 6, RDdata = 1e8dcd3d, RegWrite = 1, RS1data = 00000000, RS2data = xxxxxxxx
@225: RS1addr = 0, RS2addr = 6, RDaddr = 6, RDdata = 1e8dcd3d, RegWrite = 1, RS1data = 00000000, RS2data = 1e8dcd3d
@230: RS1addr = 0, RS2addr = 6, RDaddr = 6, RDdata = 1e8dcd3e, RegWrite = 0, RS1data = 00000000, RS2data = 1e8dcd3d

@19710: RS1addr = 28, RS2addr = 31, RDaddr = 31, RDdata = e4824cca, RegWrite = 0, RS1data = b7f4306f, RS2data = e4824cc9
@19730: RS1addr = 29, RS2addr = 30, RDaddr = 29, RDdata = e4d820c9, RegWrite = 1, RS1data = 4ad39595, RS2data = be43ea7c
@19735: RS1addr = 29, RS2addr = 30, RDaddr = 29, RDdata = e4d820c9, RegWrite = 1, RS1data = e4d820c9, RS2data = be43ea7c
@19740: RS1addr = 29, RS2addr = 30, RDaddr = 30, RDdata = 5a3761b4, RegWrite = 1, RS1data = e4d820c9, RS2data = be43ea7c
@19745: RS1addr = 29, RS2addr = 30, RDaddr = 30, RDdata = 5a3761b4, RegWrite = 1, RS1data = e4d820c9, RS2data = 5a3761b4
@19750: RS1addr = 29, RS2addr = 30, RDaddr = 30, RDdata = 5a3761b5, RegWrite = 0, RS1data = e4d820c9, RS2data = 5a3761b4
@19770: RS1addr = 29, RS2addr = 31, RDaddr = 29, RDdata = 6d48a5da, RegWrite = 1, RS1data = e4d820c9, RS2data = e4824cc9
@19775: RS1addr = 29, RS2addr = 31, RDaddr = 29, RDdata = 6d48a5da, RegWrite = 1, RS1data = 6d48a5da, RS2data = e4824cc9
@19780: RS1addr = 29, RS2addr = 31, RDaddr = 31, RDdata = d6aea8ad, RegWrite = 1, RS1data = 6d48a5da, RS2data = e4824cc9
@19785: RS1addr = 29, RS2addr = 31, RDaddr = 31, RDdata = d6aea8ad, RegWrite = 1, RS1data = 6d48a5da, RS2data = d6aea8ad
@19790: RS1addr = 29, RS2addr = 31, RDaddr = 31, RDdata = d6aea8ae, RegWrite = 0, RS1data = 6d48a5da, RS2data = d6aea8ad
@19810: RS1addr = 30, RS2addr = 31, RDaddr = 30, RDdata = 6fcff1df, RegWrite = 1, RS1data = 5a3761b4, RS2data = d6aea8ad
@19815: RS1addr = 30, RS2addr = 31, RDaddr = 30, RDdata = 6fcff1df, RegWrite = 1, RS1data = 6fcff1df, RS2data = d6aea8ad
@19820: RS1addr = 30, RS2addr = 31, RDaddr = 31, RDdata = 06b0e30d, RegWrite = 1, RS1data = 6fcff1df, RS2data = d6aea8ad
@19825: RS1addr = 30, RS2addr = 31, RDaddr = 31, RDdata = 06b0e30d, RegWrite = 1, RS1data = 6fcff1df, RS2data = 06b0e30d
@19830: RS1addr = 30, RS2addr = 31, RDaddr = 31, RDdata = 06b0e30e, RegWrite = 0, RS1data = 6fcff1df, RS2data = 06b0e30d
all correct!
Registers_tb.v:97: $finish called at 1984000 (10ps)
```

- Waveforms (excerpt):

